

HW3 Report

b09902004 資工二 郭懷元

Refs:

<https://hackmd.io/@sysprog/Byzoigglb>

ALU

unsigned arithmetic

- Overflows in `Signed Add` and `Signed Sub` are detected with an additional bit in the front.
- Overflows in `Signed Mul` are detected by using a 64-bit register to store the full result, then check if that overflows 32 bits.

signed arithmetic

- Overflows in `Unsigned Add` are detected by $(a_msb \sim b_msb) \& (a_msb \wedge o_msb)$.
- Overflows in `Unsigned Sub` are detected by $(a_msb \wedge b_msb) \& (a_msb \wedge o_msb)$.
- Overflows in `Unsigned Mul` are detected by using a 64-bit register to store the full result, then check if that's out of range.

bit operations

- `BitReverse` :

```
o_data_w = ((o_data_w&32'hffff0000)>>16|(o_data_w&32'h0000ffff)<<16);
o_data_w = ((o_data_w&32'hff00ff00)>>8|(o_data_w&32'h00ff00ff)<<8);
o_data_w = ((o_data_w&32'hf0f0f0f0)>>4|(o_data_w&32'h0f0f0f0f)<<4);
o_data_w = ((o_data_w&32'hcccccccc)>>2|(o_data_w&32'h33333333)<<2);
o_data_w = ((o_data_w&32'haaaaaaaa)>>1|(o_data_w&32'h55555555)<<1);
```

This algorithm use bit masks to achieve reversing.

- Other operations are done naively.

FPU

Add

- Because the maximum right shift amount possible here is 253(0xFE-0x01), I use a 277-bit register to store fractions.
- The hardware can be split into 4 parts:
 1. Shift the input fraction with smaller exponent.
 2. Add or subtract fractions and calculate sign according to their sign.
 - An additional bit is used for overflow detection, which is used in normalizing.
 3. Normalize output.
 4. Round to nearest even and re-normalize if needed.

Mul


- The hardware can be split into 5 parts:
 1. Add exponents
 2. Multiply fractions
 - Because the calculation here is:

$$(1.\text{frac}_1 \times 2^{23}) \times (1.\text{frac}_b \times 2^{23}) = 1.\text{frac}_o \times 2^{46}$$

I use a 47-bit register to store output fraction, and a 1-bit register for overflow.

3. Normalize output.
4. Calculate sign.
5. Round to nearest even and re-normalize if needed.

CPU

 

I define 16 states for CPU. And at every rising edge of clock, the CPU enters the next stage.

- Stage 0
 - Write data to register if needed.
 - Prepare data for fetching instruction.
- Stage 1
 - `o_i_valid_addr` is toggled and `o_i_addr` is set.
- Stage 2-6
 - Wait for memory IO.
- Stage 7
 - Decode the instruction. Extend immediate to 64 bits.
 - Do the arithmetic needed.
 - Compare for branching.
 - Prepare data for data memory IO.
- Stage 8
 - `o_d_*` ports have values set.
- Stage 9-15
 - Wait for memory IO.
 - On stage 15, calculate `pc` 's next value.

A rough block diagram of my design is below:

